Tanta University
Faculty of engineering
Electrical Power and Machines engineering department
Principles of Energy Conversion Course

Sheet (2) ..... D.C. Motors

1) A 4 pole, lap wound, D.C. motor has 540 conductors. Its speed is found to be 1000 r.p.m. when it is made to run light. The flux per pole is 25 mWb. It is connected to 230 V D.C. supply. The armature resistance is 0.8 Ω. Calculate:
   i) Induced e.m.f. ii) Armature current iii) Stray losses iv) Lost torque

2) A d.c. shunt motor runs at a speed of 1000 r.p.m. on no load taking a current of 6 A from the supply, when connected to 220 V d.c. supply. Its full load current is 50 A. Calculate its speed on full-load. Assume R_a=0.3 Ω and R_{sh}=110 Ω.

3) A d.c. series motor is running with a speed of 800 r.p.m. while taking a current of 20 A from the supply. If the load is changed such that the current drawn by the motor is increased to 50 A, calculate the speed of the motor on new load. The armature and series field winding resistances are 0.2 Ω and 0.3 Ω respectively. Assume the flux produced is proportional to the current. Assume supply voltage as 250 V.

4) A 250 V d.c. shunt motor has a shunt field resistance of 200 Ω and an armature resistance of 0.3 Ω. For a given load, motor runs at 1500 r.p.m. drawing a current of 22 A from the supply. If a resistance of 150 Ω is added in series with the field winding, find the new armature current and the speed. Assume load torque constant and magnetization curve to be linear.

5) A d.c. series motor runs at 500 r.p.m. on 220 V supply drawing a current of 50 A. the total resistance of the machine is 0.15 Ω, calculate the value of the extra resistance to be connected in series with the motor circuit that will reduce the speed to 300 r.p.m. The load torque being half of the previous value. Assume flux proportional to the current.

6) A 500 V d.c. shunt motor runs at its normal speed of 250 r.p.m. when the armature current is 200 A. The armature resistance is 0.12 Ω. Calculate the speed when a resistance is inserted in the field reducing the shunt field current to 80% of the normal value and the armature current is 100 A.

Best wishes
Course committee:
Dr. Abd Al-Wahab Hasan
Eng. Mohamed Gamal
Eng. Kotb Mohamed

Electrical Motor

①

فكرة العمل: عندما يمر موصل تيار كهربي في مجال مغناطيسي يتأثر هذا الموصل بقوة تؤدي إلى تحريكه هذه القوة يعبر عنها كالتالي:

$F = B l I$ (N)

B: Flux density, l: length of conductor, I: current carrying conductor

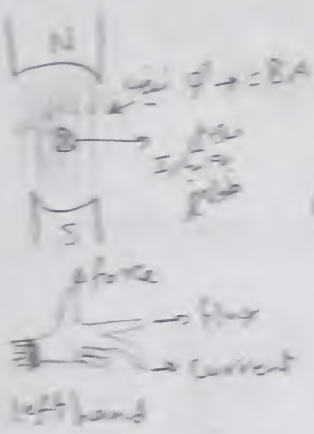

- يتم تحديد إتجاه القوة بتطبيق قاعدة اليد اليسرى
- الإبهام يمثل إتجاه القوة
- السبابة يمثل إتجاه الفيض
- الوسطى يمثل إتجاه التيار

- يعكس إتجاه دوران الموتور بتعكس أحد المجالين
- أو تغيير إتجاه التيار المار في الموصل

- يتولد القوة الدافعة العكسية Back EMF في الموتور بالعلاقة الآتية $E_b = \frac{\phi Z N}{60 A}$ وتكون هذه القوة دائماً عكس إتجاه التيار المسبب لتكوينها حسب قاعدة لينز

- تمثيل معادلة الموتور:

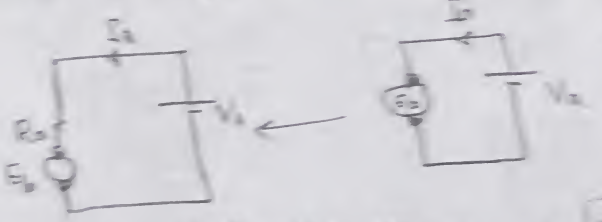

$\therefore V_a = I_a R_a + E_b + V_{brush}$ $\therefore I_a = \frac{V_a - E_b}{R_a}$

وتختلف المعادلة من تكوينها على حسب نوع الموتور

- أنواع الـ DC Motor:

مع كتابة معادلات كل نوع أثناء الرسم

- Separately excited
- Shunt
- Series
- Compound < short shunt / long

- Motor Power Equation:

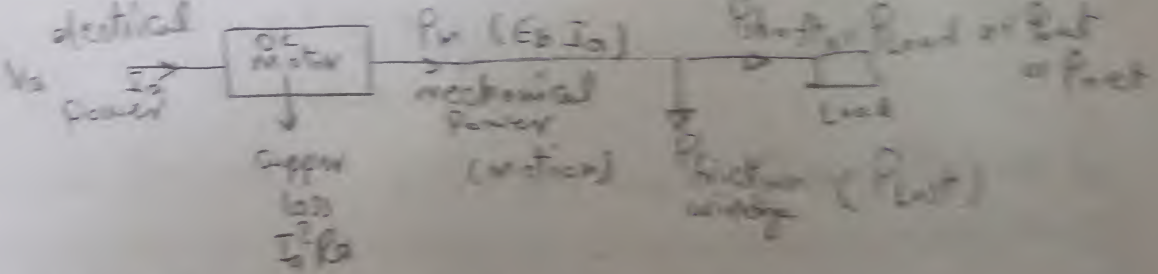

$V_a = E_b + I_a R_a \times I_a \therefore V_a I_a = E_b I_a + I_a^2 R_a$

$V_a I_a$ ← Total net elec. power

$E_b I_a$ ← Gross mechanical Power (P_m)

$I_a^2 R_a$ ← Copper loss / Armature

So P_{in} = Power i/p - Arm. Copper loss

معادلة العزم في الموتور : Torque Equ.

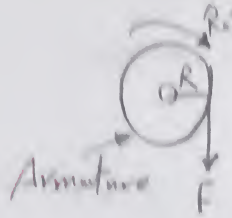

if the motor rotate with N (rpm) speed

so angular speed $\omega = \frac{2\pi N}{60}$ rad/sec.

work done in one revolution $\rightarrow W$

$W = F \times$ distance in one revolution $\rightarrow$ كيف $2\pi R$

$W = F \times 2\pi R$

القدرة المتولدة : Power developed or gross mech. Power

$P_a = \frac{W}{t} = \frac{F \times 2\pi R}{\text{زمن دورة}} = \frac{F \times 2\pi R}{(\frac{60}{N})} = F \times R \times (\frac{2\pi N}{60})$

where $\omega = \frac{2\pi N}{60}$, $T = F \times R$ العزم المتولد

$\therefore P_a = T_a . \omega$

P_a ← gross mech. → T_a gross Torque or Arm. Torque or developed Torque

$\therefore E_b I_a = T_a \cdot \frac{2\pi N}{60}$

$\frac{\phi P N Z}{60 A} I_a = T_a \frac{2\pi N}{60}$

$\therefore T_a = \frac{1}{2\pi} . I_a . \phi . \frac{PZ}{A}$

Torque Equation of D.C motor ←

$$\therefore T_a = 0.159\, \phi\, I_a \frac{PZ}{A} \quad (N.m)$$

أنواع العزوم في الموتور .

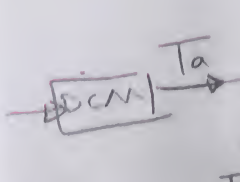

Called useful Torque

$\therefore T_a = T_f + T_{sh}$

$\therefore P_{out} = T_{sh} . \omega$

Net output power

العزم عند no-load

at No-load $\rightarrow T_{sh} = T_{Load} = 0 = P_{out}$

لكن الموتور يدور بدون حمولة No ، يسحب تيار I_{ao} ليغذي الضياعات الموجودة في الآلة فقط

وبالتالي تتولد E_{bo}

وبما أن ϕ موجود و I_a موجود

$\therefore$ ينتج عزم عند اللاحمل

$\therefore I_{ao} \phi \propto T_{ao}$ الذي يسبب هذا العزم

③

$\therefore T_{ao} \propto \phi I_{ao}$

$\therefore T_a = T_f + T_h \xrightarrow{\text{so}} \therefore \boxed{T_{ao} = T_f}$

∴ العزم الناتج عند الاحمال هو العزم المفقود على الـ shaft

So Power developed $\boxed{E_{bo} I_{ao}}$ = friction, windage, iron losses

Called stray losses

$$\therefore T_{ao} = T_f = \frac{P_{ao}}{\omega_o} = \frac{E_{bo} I_{ao}}{\left(\frac{2\pi N_o}{60}\right)} \quad N.m$$

---

problem ① $P = 4$, $A = P = 4$, $Z = 540$, $N = 1000$ rpm (when run light) N_o

$\phi = 25 * 10^{-3}$ Wb, $V_a = 230$ V, $R_a = 0.8\,\Omega$

Req. E_{bo}, I_{ao}, P_{stray}, T_f

الحل

$N_o \longrightarrow 1000$ rpm ∴ Motor operate at no-load

$$\therefore E_{bo} = \frac{\phi P N_o Z}{60 A} = \boxed{225\ V}$$

$\therefore V_a = E_b + I_a R_a \longrightarrow V_a = E_{bo} + I_{ao} R_a$

$$\therefore I_{ao} = \frac{230 - 225}{0.8} = \boxed{6.25\ A}$$

$P_{stray} = E_{bo} I_{ao} = \boxed{1406.25\ W}$

$$T_f = \frac{P_{stray}}{\omega_o} = \frac{P_{ao}}{\omega_o} = \frac{1406.25}{\left(\frac{2\pi * 1000}{60}\right)} = \boxed{13.428\ N.m}$$

(4)

problem (2) $N_o = 1000$ rpm , $I_{Lo} = 6A$, $V_o = 220V$, $I_{f.L} = 50A$

$N_{f.L} = ?$, $R_a = 0.3\Omega$, $R_{sh} = 110\Omega$

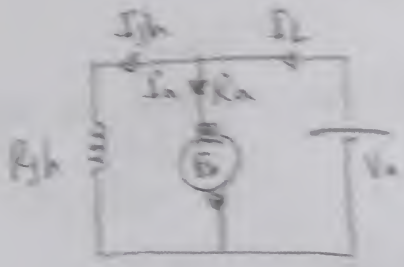

Ms1

→ at no-load $I_{bo} = 6A$

$\therefore I_{Lo} = I_{ao} + I_{sh}$, $I_{sh} = \frac{220}{110} = 2A$

$\therefore \boxed{I_{ao} = 6 - 2 = 4A}$

$\therefore V_o = E_{bo} + I_{ao} R_a$

$\therefore \boxed{E_{bo} = 218.8V}$

→ at full load I_{sh} → const.

$I_{L f.L} = 50 = I_{a f.L} + I_{sh}$

$\therefore I_{a f.L} = 50 - 2 = \boxed{48A}$

$\therefore E_{b f.L} = V_o - I_{a f.L} R_a = \boxed{205.6V}$

$\therefore E_b = \frac{\phi P N Z}{60A}$ $\therefore N \propto \frac{E_b}{\phi}$ $\therefore N = K \frac{E_b}{\phi}$

$\therefore \frac{N_1}{N_2} = \frac{(E_{b1})/(\phi_1)}{(E_{b2})/(\phi)_L}$ but ϕ_1 is const → shunt motor

$\therefore \frac{N_1}{N_2} = \frac{E_{b1}}{E_{b2}}$ $\therefore \frac{N_{n.L}}{N_{f.L}} = \frac{E_{bo}}{E_{b f.L}}$

$\therefore N_{f.L} = \frac{E_{b f.L}}{E_{bo}} \cdot N_{n.L}$

$\therefore \boxed{N_{f.L} = 939.67 \text{ r.p.m}}$ #

(5)

Prob (3) series Motor $N_1 = 800$ rpm , $I_{L_1} = 20$ A

$I_{L_2} = 50$ A , $N_2 = ?$, $R_a = 0.2\Omega$, $R_{se.} = 0.3\Omega$

$\phi \propto I_a, I_L$, $V_a = 250$ V

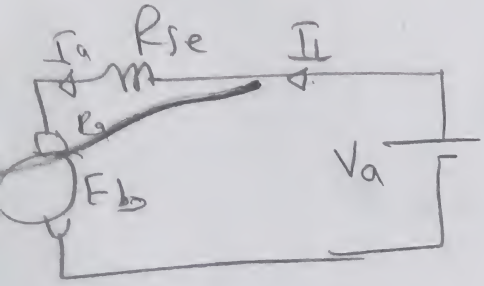

Sol

→ For Load ① $N_1 = 800$ rpm

$I_{a1} = I_{L1} = 20$ A

$\therefore V_a = E_b + I_a (R_a + R_{se.})$

$\therefore E_{b1} = V_a - I_{a1} (R_a + R_{se})$

$\therefore \boxed{E_{b1} = 240 \text{ V}}$

→ for Load ② $I_{a2} = I_{L2} = 50$ A $\therefore E_{b2} = V_a - I_{a2}(R_a + R_{se})$

$\therefore N \propto \frac{E_b}{\phi}$, $\phi \propto I_a, I_L$ $\boxed{E_{b2} = 225}$

$\therefore \frac{N1}{N_2} = \frac{(E_{b1}/I_{a1})}{(E_{b2}/I_{a2})}$ $\therefore \frac{N1}{N_2} = \frac{E_{b1} . I_{a2}}{E_{b2} . I_{a1}}$

$\therefore N_2 = N_1 . \frac{E_{b2} . I_{a2}}{E_{b1} . I_{a1}} = 800 * \frac{225 * 20}{240 * 50}$

$\therefore \boxed{N_2 = 300 \text{ rpm}}$ #

(6)

problem 2 $V_a = 250V$ shunt , $R_{sh_1} = 200\Omega$, $R_a = 0.3\Omega$

$N_1 = 1500 rpm$, $I_{L_1} = 22A$, $R_{sh_{new}} = 200 + 150\Omega$ $\rightarrow$ $I_{a_{new}} = ?$

$N_{2_{new}} = ?$ Assume load torque = const.

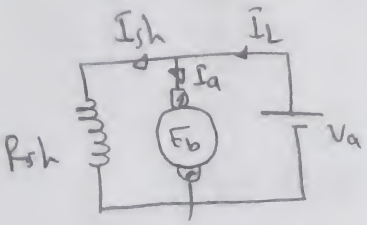

$\rightarrow$ for the first load

$I_{L_1} = 22A = I_{a_1} + I_{sh_1}$

$I_{sh_1} = \frac{V_a}{R_{sh_1}} = \frac{250}{200} = 1.25A$

$\therefore \boxed{I_{a_1} = 20.75A}$ $\therefore E_{b_1} = V_a - I_{a_1} R_a$

$\therefore E_{b_1} = 250 - 20.75 \times 0.3 = \boxed{243.775V}$

$\because T_a = 0.159 \phi I_a \cdot \frac{PZ}{A}$ $\therefore T_a \propto \phi I_a$, $\phi \propto I_{sh}$

$\therefore T_a \propto I_{sh} I_a$ $\therefore \frac{T_1}{T_2} = \frac{I_{sh_1} \cdot I_{a_1}}{I_{sh_2} \cdot I_{a_2}}$

$\because$ Said Load torque = Const $\rightarrow$ $\therefore T_1 = T_2$

$\therefore I_{sh_1} I_{a_1} = I_{sh_2} I_{a_2}$

$I_{sh_2} = \frac{V_a}{R_{sh_{new}}} = \frac{250}{200+150} = \boxed{0.7142A}$

$\therefore I_{a_2} = \frac{I_{sh_1} I_{a_1}}{I_{sh_2}} = \boxed{36.3125A}$

$\therefore E_{b_2} = V_a - I_{a_2} R_a$

$\therefore \boxed{E_{b_2} = 239.1062V}$

$\because N \propto \frac{E_b}{\phi}$ $\therefore \frac{N_1}{N_{2_{new}}} = \frac{E_{b_1}}{E_{b_2}} \cdot \frac{I_{sh_2}}{I_{sh_1}}$

$\therefore \boxed{N_{2_{new}} = 2575.03 rpm}$ #

Problem (5)

series at $N_1 = 500$ rpm , $V_a = 220$V , $I_{L_1} = 50$A

$(R_a + R_{se.}) = 0.15\,\Omega$, $R_{ext.} = ?$ $\rightarrow N_2 = 300$ r.p.m

$T_{L_2} = \frac{1}{2} T_{L_1}$, $\phi \propto I_a, I_L$

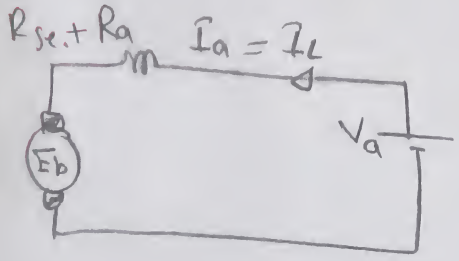

(1)

$\therefore V_a = E_{b_1} + I_{a_1}(R_a + R_{se.})$

$I_{a_1} = I_{L_1} = 50$A

$\therefore E_b = 220 - 50(0.15) = \boxed{212.5\text{V}}$

$V_a = E_{b_2} + I_{a_2}(R_a + R_{se.} + R_{ext.})$

for computing I_{a_2}

$\therefore T \propto \phi I_a$, $\phi \propto I_a$ $\therefore T \propto I_a^2$

$\therefore \frac{T_1}{T_2} = \frac{I_{a1}^2}{I_{a2}^2} \rightarrow \frac{T_1}{\frac{1}{2}T_1} = \frac{(50^2)}{I_{a2}^2}$ $\therefore \boxed{I_{a2} = 35.355\,A}$

$\therefore V_a = E_{b2} + 35.355(0.15 + R_{ext.})$

$V_a \downarrow 220$

for computing E_{b2}

$\because N \propto \frac{E_b}{\phi}$ $\therefore \frac{N_1}{N_2} = \frac{E_{b1}}{E_{b2}} \cdot \frac{I_{a2}}{I_{a1}}$

$\therefore \frac{500}{300} = \frac{212.5 * 35.355}{E_{b2} * 50}$ $\therefore \boxed{E_{b2} = 90.0279\text{V}}$

$\therefore 220 = 90.0279 + 35.355(0.15 + R_{ext.})$

$\therefore \boxed{R_{ext.} = 3.526\,\Omega}$ ✱

(8) problem (6) $V_a = 500V$ shunt $N_1 = 250$ rpm $\rightarrow I_{a1} = 200A$, $R_a = 0.12\Omega$

$N_2 = ?$ $I_{sh2} = 80\%\ I_{sh1} \rightarrow I_{a2} = 100\ A$

$$\therefore \frac{N_1}{N_2} = \frac{E_{b1}}{E_{b2}} \cdot \frac{I_{sh2}}{I_{sh1}} \rightarrow 0.8\ \frac{I_{sh1}}{I_{sh1}}$$

$$E_{b1} = V_a - I_{a1} R_a = 500 - 200 * 0.12 = 476V$$

$$E_{b2} = V_a - I_{a2} R_a = 500 - 100 * 0.12 = 488V$$

$$\therefore \frac{250}{N_2} = \frac{476}{488} * 0.8 \quad \therefore N_2 = 320.378 \text{ rpm} \ \#$$